


$$\begin{array}{r} A \\ + B \\ \hline C \quad S \end{array}$$

(b) 功能

註: $S = \text{sum} = \text{和}$
 $C = \text{carry} = \text{進位}$

輸入		輸出	
A	B	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

(c) 真值表

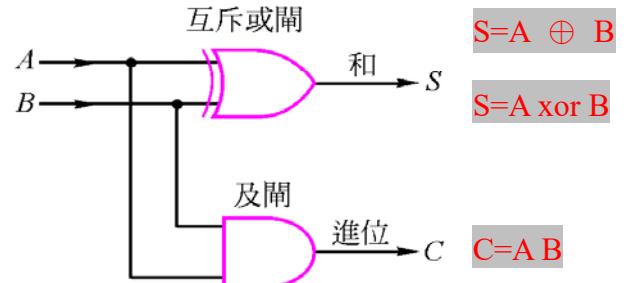

(d) 電路圖

圖 4-3 一位元之二進位半加器

半加器程式(1)

half_add.vhd

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;
use ieee.std_logic_arith.all;
--*****
entity Half_add is
    port ( A,B : in std_logic;
           S,C : out std_logic );
end Half_add;
--*****
architecture A_Boolean of Half_add is
begin
    S <= A xor B ;
    C <= A and B ;
end A_Boolean ;
```

半加器程式(2)

add_1.vhd

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;
use ieee.std_logic_arith.all;
--*****
entity add_1 is
port(
    a,b      : in std_logic_vector(0 to 0);
    s,c      : out std_logic );
end add_1;
--*****
architecture arch of add_1 is
signal temp : std_logic_vector(1 downto 0);
begin
    temp<= "00"+a + b;
    s    <= temp(0);
    c    <= temp(1);
end arch;
```

須為
vector

◆建立自己的元件庫

●先建立存放自建元件之資料夾

c:\maxplus2\max2lib\mylib

●新增元件庫

Option→User Libraries

●創造元件符號

File→Create Default Symbol

◆ 汇流排的使用

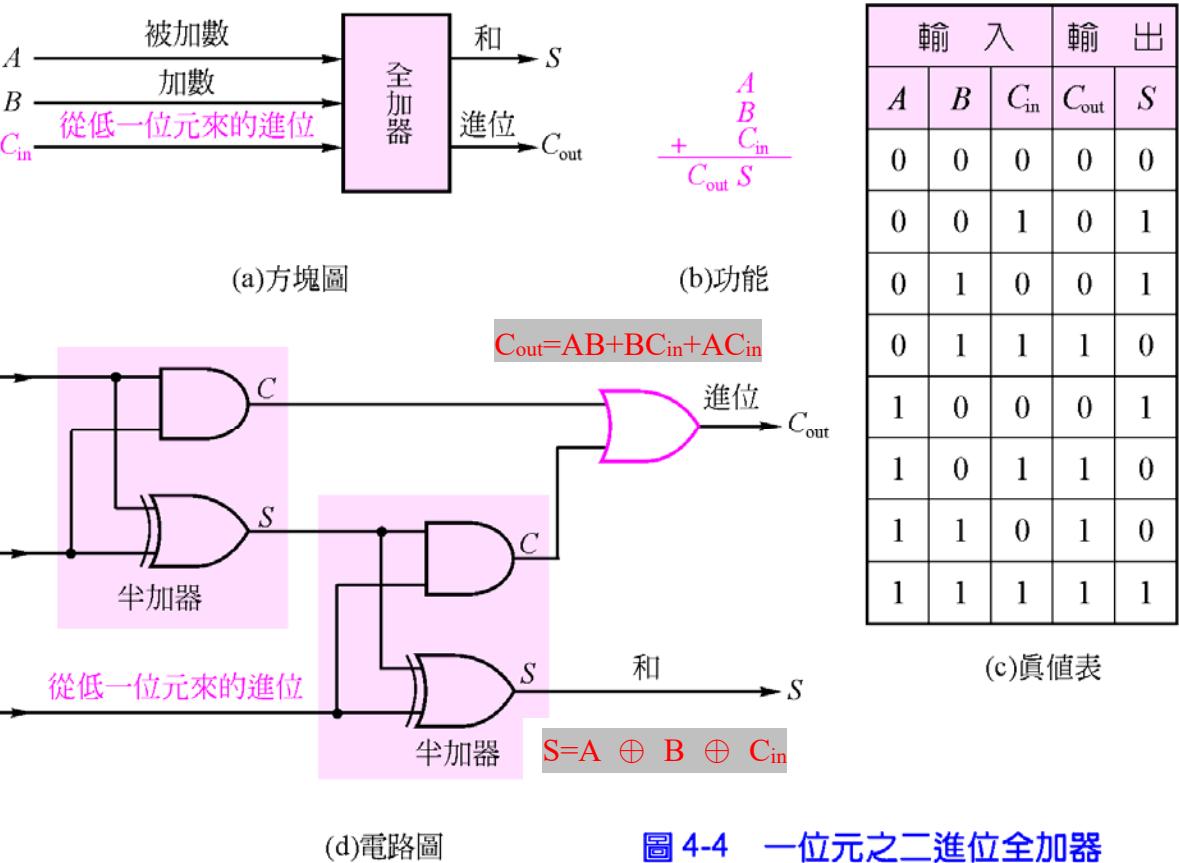


圖 4-4 一位元之二進位全加器

全加器程式(1)-布林式

full_add.vhd

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;
use ieee.std_logic_arith.all;
--*****
entity Full_add is
    port ( Ai,Bi,Ci      : in  std_logic;
           So,Co       : out std_logic );
end Full_add;
--*****
```

```
architecture A_Boolean of Full_add is
begin
    So <= Ai xor Bi xor Ci ;
    Co <= (Ai and Bi) or (Ai and Ci) or (Bi and Ci) ;
end A_Boolean ;
```

全加器程式(2)-運算式

add_1.vhd

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;
use ieee.std_logic_arith.all;
entity add_1 is
port(
    a,b,ci      :in std_logic_vector(0 to 0);
    s,c       :out std_logic);
end add_1;
```

須為 vector

```
architecture arch of add_1 is
signal temp : std_logic_vector(1 downto 0);
--內部訊號，不會出現在實體外部接線上
begin
    begin
        temp<= "00"+a + ci + b;
        s    <= temp(0);--temp(0)為 temp 低位元
        c    <= temp(1); --temp(1)為 temp 高位元
    end arch;
```


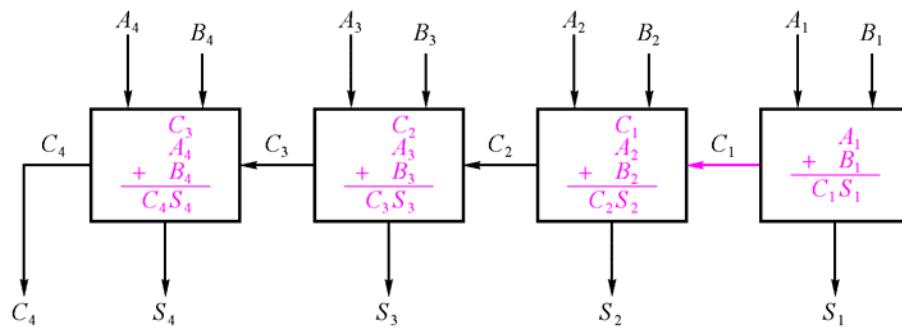


圖 4-5 4 位元加法器之概念圖

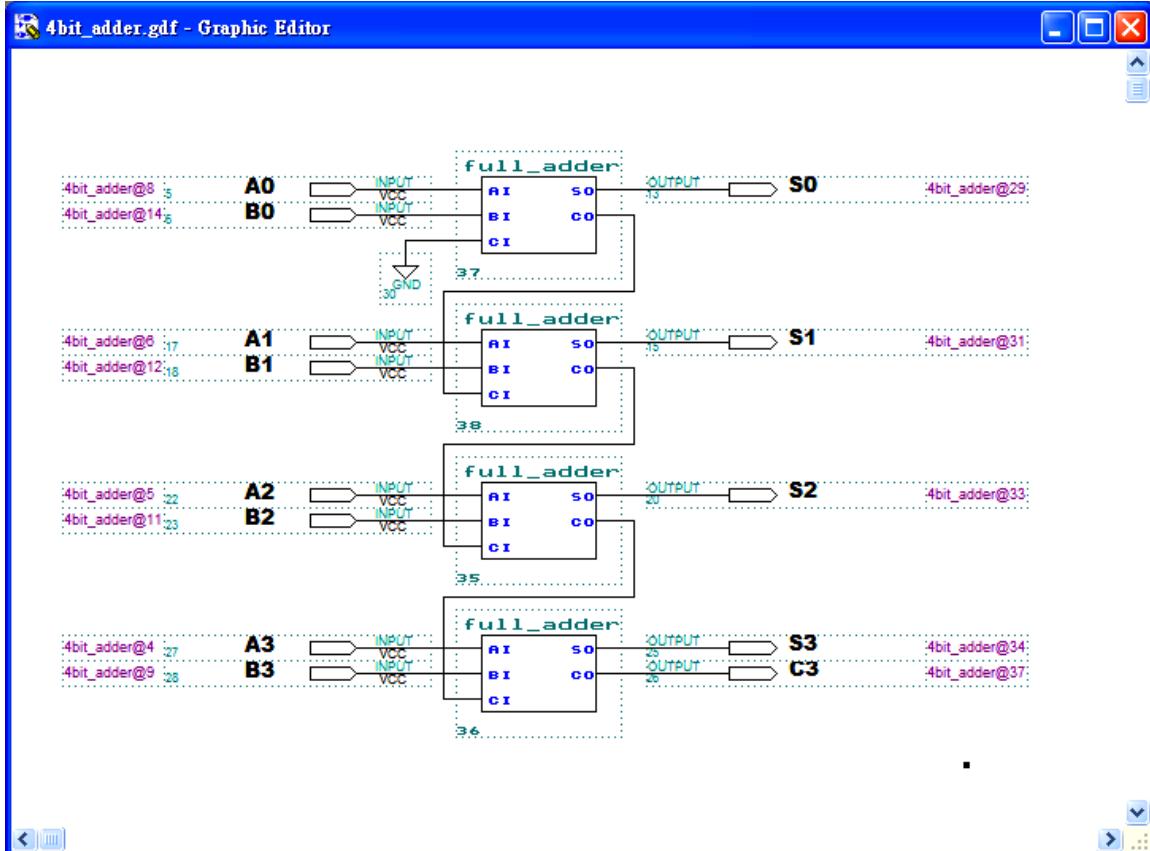

用 component 與 port map 的敘述方法描述電路

語法格式

component 元件(程式)名稱 --此一元件(程式)儲存位置須與本程式在同一目錄下

port(

 訊號 1(電路腳位名稱):I/O 屬性 資料型態;

 訊號 2(電路腳位名稱):I/O 屬性 資料型態;

 :

 :

);

end component;

四位元加法器-依電路圖方式

add_4bit.vhd

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;
use ieee.std_logic_arith.all;
--*****  
entity Add_4bit is
  port ( A,B : in std_logic_vector(3 downto 0);
         S      : out std_logic_vector(3 downto 0);
         Cout : out std_logic );
end Add_4bit;  
--*****  
architecture A_port_map of Add_4bit is
  signal C1,C2,C3 : std_logic ;
component Half_add--公用元件名稱
  port ( A,B : in std logic;
         S,C : out std logic );
end component;  
component Full_add--公用元件名稱
  port ( Ai,Bi,Ci : in std logic ;
         So,Co    : out std logic );
end component;  
begin
  U1 : Half_add  port map (A(0),B(0),S(0),C1);
  U2 : Full_add  port map (A(1),B(1),C1,S(1),C2);
  U3 : Full_add  port map (A(2),B(2),C2,S(2),C3);
  U4 : Full_add  port map (A(3),B(3),C3,S(3),Cout);
end A_port_map ;  
--位置對應方式為不使用”=>”符號，所以一定要依照  
公用元件中 port 內宣告的 I/O 順序為對應之順序  
--使用名稱對應”=>”
--U1:Half_add  port map
  (A=>A(0),B=>B(0),S=>S(0),C=>C1);
--U2:Full_add  port map
  (Ai=>A(1),Bi=>B(1),Ci=>C1,So=>S(1),Co=>C2);
```

半加器程式(1)

half_add.vhd

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;
use ieee.std_logic_arith.all;
--*****  
entity Half_add is
  port ( A,B : in std logic;
         S,C : out std logic );
end Half_add;  
--*****  
architecture A_Boolean of Half_add is
begin
  S <= A xor B ;
  C <= A and B ;
end A_Boolean ;
```

全加器程式(1)-布林式

full_add.vhd

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;
use ieee.std_logic_arith.all;
--*****  
entity Full_add is
  port ( Ai,Bi,Ci : in std logic;
         So,Co    : out std logic );
end Full_add;  
--*****  
architecture A_Boolean of Full_add is
begin
  So <= Ai xor Bi xor Ci ;
  Co <= (Ai and Bi) or (Ai and Ci) or (Bi and Ci) ;
end A_Boolean ;
```


四位元加法器 2-使用算術運算

add_4bit_1.vhd

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;
use ieee.std_logic_arith.all;
--*****
```

entity Add_4bit_1 is
port (A,B : in std_logic_vector(3 downto 0);
 S : out std_logic_vector(3 downto 0);
 Cout : out std_logic);
end Add_4bit_1;
--*****

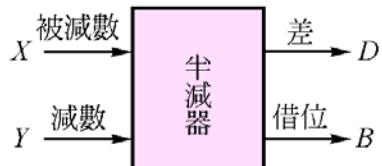architecture A_arith of Add_4bit_1 is
signal Temp : std_logic_vector(4 downto 0) ;
--signal 內部訊號宣告,宣告為標準邏輯向量,位於 architecture 與 begin 之間
begin
 Temp <= ('0' & A) + B ; --temp<=a+b;
 S <= Temp(3 downto 0);
 Cout <= Temp(4);
end A_arith ;



(a)方塊圖


$$\begin{array}{r} X \\ - Y \\ \hline B \quad D \end{array}$$

(b)功能

註: $D = \text{difference} = \text{差}$
 $B = \text{borrow} = \text{借位}$

輸入		輸出	
X	Y	B	D
0	0	0	0
0	1	1	1
1	0	0	1
1	1	0	0

(c)真值表

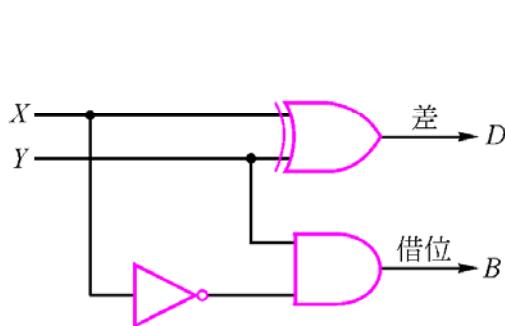

(d)電路圖

$$\begin{aligned} D &= X \oplus Y \\ &= X \text{ xor } Y \end{aligned}$$

$$B = X'Y$$

圖 5-1 一位元的二進位半減器

Half_sub.vhd

```

library ieee ;
use ieee.std_logic_1164.all ;
use ieee.std_logic_unsigned.all ;
use ieee.std_logic_arith.all ;
--*****entity Half_sub is
port ( A,B      : in  std_logic ;
       Do,Bo : out std_logic ) ;
end Half_sub ;
--*****
architecture A_boolean of Half_sub is
begin
  Do <= A xor B;
  Bo <= (not A) and B ;
end A_boolean ;

```

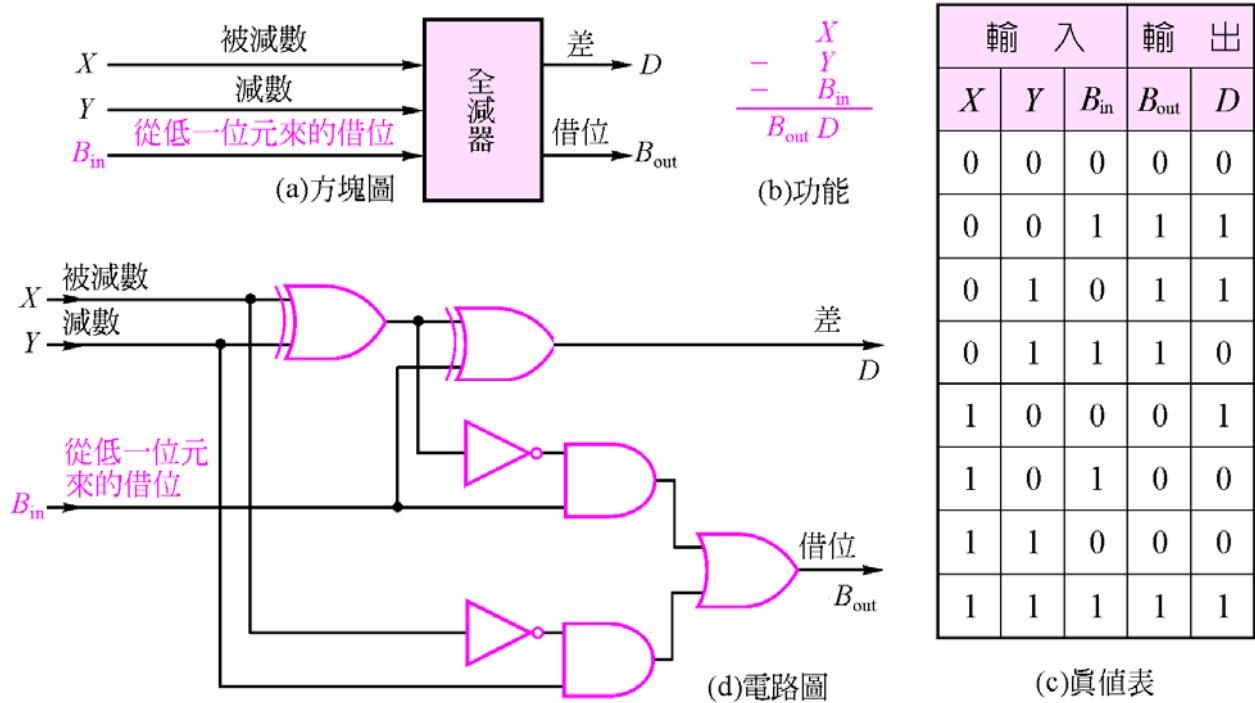


圖 5-2 一位元之二進位全減器

$$\text{差 } D(a,b,B_i) = \sum(1,2,4,7) = a'b'bi + a'bbi' + ab'bi' + abbi$$

$$\text{借位 } B(a,b,B_i) = \sum(1,2,3,7) = a'b'bi + a'bbi' + a'bbi + abbi$$

(1) Full_sub.vhd—布林式

```

library ieee ;
use ieee.std_logic_1164.all ;
use ieee.std_logic_unsigned.all ;
use ieee.std_logic_arith.all ;
--*****entity Full_sub is
port ( A,B,Bi : in std_logic;
       Do,Bo : out std_logic ) ;
end Full_sub ;
--*****
architecture A_table of Full_sub is
begin
  Do <= ((not A) and (not B) and Bi) or
        ((not A) and B and (not Bi)) or
        (A and (not B) and (not Bi)) or
        (A and B and Bi) ;
  Bo <= ((not A) and (not B) and Bi) or
        ((not A) and B and (not Bi)) or
        ((not A) and B and Bi)      or
        (A and B and Bi) ;
end A_table ;

```

使用 whenelse 描述敘述，其語法格式為

[輸出]訊號	<=	輸出邏輯狀態 1	when	判斷條件 1	else
		[輸出邏輯狀態 2	when	判斷條件 2	else]
		[.....]			
		輸出邏輯狀態 N;			

(2) Full_sub_1.vhd -- 使用 when ...else

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;
use ieee.std_logic_arith.all;
--*****
entity Full_sub_1 is
    port ( A,B,Bi : in std_logic;
           Do,Bo : out std_logic );
end Full_sub_1;
--*****
architecture A_when_else of Full_sub_1 is
begin
    Do <= '1' when (A='0' and B='0' and Bi='1') else
        '1' when (A='0' and B='1' and Bi='0') else
        '1' when (A='1' and B='0' and Bi='0') else
        '1' when (A='1' and B='1' and Bi='1') else
        '0';
    Bo <= '1' when (A='0' and B='0' and Bi='1') else
        '1' when (A='0' and B='1' and Bi='0') else
        '1' when (A='0' and B='1' and Bi='1') else
        '1' when (A='1' and B='1' and Bi='1') else
        '0';
end A_when_else ;
```

Full_sub_2.vhd-- 使用 when ...else

```
library ieee ;
use ieee.std_logic_1164.all ;
use ieee.std_logic_unsigned.all ;
use ieee.std_logic_arith.all ;
--*****
entity Full_sub_2 is
    port ( A,B,Bi : in  std_logic;
           Do,Bo  : out std_logic ) ;
end Full_sub_2 ;
--*****
architecture A_when_else of Full_sub_2 is
    signal Temp : std_logic_vector( 2 downto 0 ) ;
begin
    Temp <= A & B & Bi ;
    Do <= '1' when Temp="001" else
        '1' when Temp="010" else
        '1' when Temp="100" else
        '1' when Temp="111" else
        '0';
    Bo <= '1' when Temp="001" else
        '1' when Temp="010" else
        '1' when Temp="011" else
        '1' when Temp="111" else
        '0';
end A_when_else ;
```

Full_sub_3.vhd-- 使用 when ...else

```
library ieee ;
use ieee.std_logic_1164.all ;
use ieee.std_logic_unsigned.all ;
use ieee.std_logic_arith.all ;
--*****
entity Full_sub_3 is
    port ( A,B,Bi  : in  std_logic;
           Do,Bo  : out std_logic ) ;
end Full_sub_3 ;
--*****
architecture A_when_else of Full_sub_3 is
    signal Temp : std_logic_vector( 2 downto 0 ) ;
    signal O_temp : std_logic_vector( 1 downto 0 ) ;
begin
    Temp <= A & B & Bi ;
    O_temp <= "11" when Temp="001" else
        "11" when Temp="010" else
        "10" when Temp="011" else
        "01" when Temp="100" else
        "11" when Temp="111" else
        "00" ;
    Do <= O_temp(0) ;
    Bo <= O_temp(1) ;
end A_when_else ;
```

使用 with.....select.....when 語法格式如下

[輸出]訊號	<=	輸出的邏輯狀態 1 when	判斷訊號的邏輯狀態 1,
		輸出的邏輯狀態 2 when	判斷訊號的邏輯狀態 2,
		[.....],	
		輸出的邏輯狀態 N	when others;

Full_sub_4.vhd--使用 with.....select.....when

```
library ieee ;
use ieee.std_logic_1164.all ;
use ieee.std_logic_unsigned.all ;
use ieee.std_logic_arith.all ;

--*****
entity Full_sub_4 is
    port ( A,B,Bi : in  std_logic;
           Do,Bo   : out std_logic ) ;
end Full_sub_4 ;
--*****

architecture A_with_select_when of Full_sub_4 is
    signal Temp : std_logic_vector( 2 downto 0 ) ;
begin
    Temp <= A & B & Bi;
    with Temp select
        Do <= '1' when "001" ,
                  '1' when "010" ,
                  '1' when "100" ,
                  '1' when "111" ,
                  '0' when others;
    with Temp select
        Bo <= '1' when "001" ,
                  '1' when "010" ,
                  '1' when "011" ,
                  '1' when "111" ,
                  '0' when others;
end A_with_select_when ;
```

補數

$$x - y = x + (-y)$$

將一正數的二進位取 2 的補數，就是其負數。

步驟： (1)先寫出該數之 2 進位數。

(2)將此 2 進位數的每個位元**反相**，此時的值稱為 1 的補數。

(3)再把 1 的補數**加 1**，即為 2 的補數。

例：10 進位 -3_{10} 的 2 的補數

因為 $3_{10} = 0011$

所以 0011

↓ 反相

1100

↓ 加 1

1101

所以得知 -3_{10} 用 2 的補數表示為 1101

例： $11 - 4 = 7$

先求 -4 的 2 的補數為

0100

↓ 反相

1011

↓ 加 1

1100

則 1011 ← 11

$+ 1100 \quad \leftarrow -4$ 的 2 的補數

10111

↑ 最高位元 0 表正數
溢位，忽略

所以答案為 $0111 = 7$

例： $9 - 21 = -12$

-21 的 2 的補數為

10101

↓ 反相

01010

↓ 加 1

01011

則 01001 ← 9

$+ 01011 \quad \leftarrow -12$ 的 2 的補數

10100

↑ 沒有進位最高位元 1 表負數

答案如為負數，需再取其 2 的補數

10100

↓ 反相

01011

↓ 加 1

01100 = 12_{10}

所以答案為 -12

運用 process 順序性敘述 與 if..then..else 敘述

Add_sub_4bit.vhd

```
library ieee ;
use ieee.std_logic_1164.all ;
use ieee.std_logic_unsigned.all ;
use ieee.std_logic_arith.all ;
--*****  
entity Add_sub_4bit is
port (
    SUB : in  std_logic;
    A,B : in  std_logic_vector(3 downto 0);
    S    : out std_logic_vector(3 downto 0);
    C3   : out std_logic
);
end Add_sub_4bit ;
--*****  
architecture ARCH of Add_sub_4bit is
begin
    signal Temp : std_logic_vector(4 downto 0);
    begin
        process(SUB,A,B)
        begin
            if SUB = '0' then
                Temp <= ( '0' & A ) + B;  ← 加法
                S <= Temp(3 downto 0);
                C3<= Temp(4);
            else
                Temp <= ('0' & A) + ( not(B) + 1 );  ←減法
                S <= Temp(3 downto 0);
                C3 <= Temp(4);
            end if;
        end process;
    end ARCH ;
```

[標名:] process(感測訊號 1,2,...)
[訊號、變數宣告]
begin
 [順序性敘述]或[指定敘述]

end process[標名];

if 判斷條件 1 then
 第一組敘述;
[elsif 判斷條件 2 then
 第二組敘述;
 :
]
else
 第 N 組敘述;
end if;

BCD 碼對共陰 7 段顯示器之解碼器

```
library ieee ;
use ieee.std_logic_1164.all ;
use ieee.std_logic_unsigned.all ;
use ieee.std_logic_arith.all ;
--*****
entity BCD_to_7seg_c is
port ( B0,B1,B2,B3    : in std_logic  ;
       Y      : out std_logic_vector(0 to 6)) ;
end BCD_to_7seg_c ;
--*****
architecture A_case_when of BCD_to_7seg_c is
signal Temp : std_logic_vector(3 downto 0) ;
begin
  Temp <= B3 & B2 & B1 & B0 ;
  process(Temp)
  begin
    case Temp is
      when "0000" => Y<= "1111110" ;
      when "0001" => Y<= "0110000" ;
      when "0010" => Y<= "1101101" ;
      when "0011" => Y<= "1111001" ;
      when "0100" => Y<= "0110011" ;
      when "0101" => Y<= "1011011" ;
      when "0110" => Y<= "0011111" ;
      when "0111" => Y<= "1110000" ;
      when "1000" => Y<= "1111111" ;
      when "1001" => Y<= "1110011" ;
      when others => Y<= "1001111" ;
    end case;
  end process;
end A_case_when ;
```

```
library ieee ;
use ieee.std_logic_1164.all ;
use ieee.std_logic_unsigned.all ;
use ieee.std_logic_arith.all ;
--*****
entity BCD_to_7seg_c_2 is
port ( BCD : in integer range 0 to 15 ;
       Y      : out std_logic_vector(0 to 6)) ;
end BCD_to_7seg_c_2 ;
--*****
architecture A_with_select_when of
BCD_to_7seg_c_2 is
begin
  with BCD select
    Y <= "1111110" when 0 ,
                  "0110000" when 1 ,
                  "1101101" when 2 ,
                  "1111001" when 3 ,
                  "0110011" when 4 ,
                  "1011011" when 5 ,
                  "0011111" when 6 ,
                  "1110000" when 7 ,
                  "1111111" when 8 ,
                  "1110011" when 9 ,
                  "1001111" when 10 to 15 ;
  end A_with_select_when ;
```

BCD 碼(0~9)(又稱 8421 碼)，以 4 個 bit 表示一個 10 進位的值。

BCD 碼加法器 BCD_add_1d.vhd

```
library ieee ;
use ieee.std_logic_1164.all ;
use ieee.std_logic_unsigned.all ;
use ieee.std_logic_arith.all ;
--*****  
entity BCD_add_1d is
port ( A,B : in std_logic_vector(3 downto 0) ;
       S    : out std_logic_vector(3 downto 0) ;
       Co   : out std_logic );
end BCD_add_1d ;
--*****  
architecture A_arith of BCD_add_1d is
signal Temp : std_logic_vector(4 downto 0) ;
begin
process(A,B)
begin
  Temp <= ('0'&A)+B ;
  if (Temp(3 downto 0)>9) OR (Temp(4)=1') then
-- if (Temp(4 downto 0)>9) then
    S <= Temp(3 downto 0)+6 ;
    Co <= '1';
  else
    S <= Temp(3 downto 0);
    Co <= '0' ;
  end if;
end process ;
end A_arith ;
```

當出現合超過 20 的數時會發生錯誤
例：9+12=21
$$\begin{array}{r} 21 \rightarrow 10101 \\ + 0110 \\ \hline 11011 \rightarrow 1011 = 11 \end{array}$$

所以 Co=1
 $S = 1011_2 = 11_{10}$

具有輸入偵誤功能之一位數 BCD 碼加法器

BCD_add_1d_1.vhd

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;
use ieee.std_logic_arith.all;
--*****  
entity BCD_add_1d_1 is
port ( A,B    : in  std_logic_vector(3 downto 0);
       S      : out std_logic_vector(3 downto 0);
       Co,E   : out std_logic );
end BCD_add_1d_1;
--*****  
architecture A_arith of BCD_add_1d_1 is
signal Temp : std_logic_vector(4 downto 0);
begin
process(A,B)
begin
  Temp <= ('0'&A)+B ;
  if (A(3 downto 0)>9) OR (B(3 downto 0)>9) then
    S <= "ZZZZ"; --大寫'Z'表示高阻抗
    Co <= 'Z';
    E <= '1'; --錯誤輸出端設定為 1
    --以下程式與上一程式相同
  elsif (Temp(3 downto 0)>9) OR (Temp(4)='1') then
    S <= Temp(3 downto 0)+6 ;
    Co <= '1';
    E <= '0';
  else
    S <= Temp(3 downto 0);
    Co <= '0';
    E <= '0';
  end if;
end process ;
end A_arith ;
```

```
if 判斷條件 1 then
  敘述區塊 1;
elsif 判斷條件 2 then
  敘述區塊 2;
elsif 判斷條件 3 then
  敘述區塊 3;
  :
else
  敘述區塊 N;
end if;
```

一位數 BCD 碼減法器

BCD_sub_1d.vhd

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;
use ieee.std_logic_arith.all;
--*****  
entity BCD_sub_1d is
port ( A,B : in std_logic_vector(3 downto 0);
       S    : out std_logic_vector(3 downto 0);
       Co   : out std_logic );
end BCD_sub_1d;
--*****  
architecture A_arith of BCD_sub_1d is
signal Temp : std_logic_vector(4 downto 0);
begin
process(A,B)
begin
  Temp <= ('0'&A)+(10-B); --減數取其 10 的補數
  if (A(3 downto 0)>9) OR (B(3 downto 0)>9) then --偵錯 A 或 B 大於 9 時
    S <= "ZZZZ"; --高阻抗
    Co <= 'Z';
  elsif (Temp(3 downto 0)>9) OR (Temp(4)='1') then
    S <= Temp(3 downto 0)+6;
    Co <= '1'; --表示 A-B 的差為正數
  else
    S <= 10-Temp(3 downto 0); --負數再取其 10 的補數
    Co <= '0'; --表示 A-B 的差為負數
  end if;
end process;
end A_arith;
```

3*3 位元乘法器

mul_3x3.vhd

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;
use ieee.std_logic_arith.all;
--*****
entity mul_3x3 is
port ( A,B : in std_logic_vector(2 downto 0);
       M : out std_logic_vector(5 downto 0) );
end mul_3x3;
--*****
architecture A_operator of mul_3x3 is
begin
  M <= A*B ;
end A_operator ;
```